

CSCIU 210 01– Computer Organization

Homework-2, Weight: 50 points

Due on Wednesday, September 19, 2018 at the beginning of the lecture (Hard Copy)

Note: You need to include your calculation details to receive full credit!

1. Draw the circuit diagram of $AC+AB+ABC'$ and also determine its truth table.


Solution:

The truth table of $AC+AB+ABC'$ is given below

| A | B | C | (Output) |
|---|---|---|----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |


$$AC+AB+ABC' = AC+AB(1+C') = AC+AB$$

Its circuit diagram is attached below

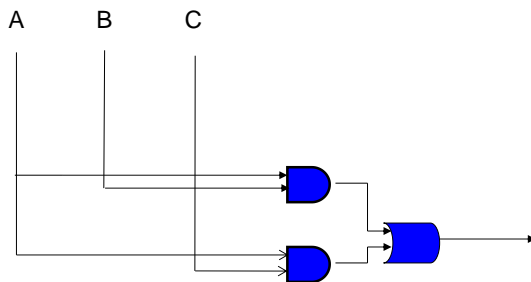

2. Determine the truth table of the circuit illustrated below


| A | B | C | (Output) |
|---|---|---|----------|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

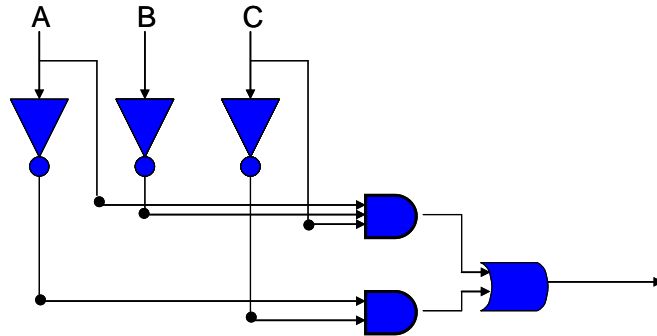

3. Based on the following truth table, draw the corresponding logic circuit diagram.

| A | B | C | F (Output) |
|---|---|---|------------|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

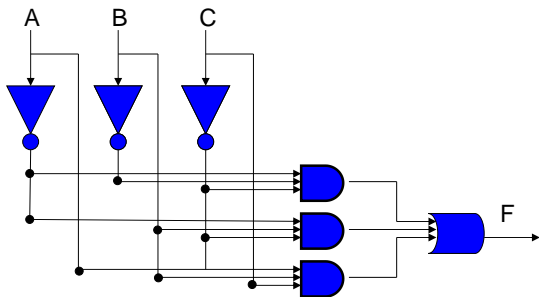$F = A'B'C' + A'BC' + ABC$. Its logic circuit diagram is attached below.



4. Convert 1011.1011_2 to a decimal number**Solution:** 11.6875_{10} **5. Convert 152.875_{10} to a binary number****Solution:** 10011000.111_2 **6. Convert 110000111101.11011101_2 to a hexadecimal number.****Solution:** $C3D.DD_{16}$ **7. Convert $12AC.EF_{16}$ to a binary number****Solution:** $0001001010101100.111011110001_2$ **8. How many bits of memory would be found in a personal computer that has the 16 MB of memory size?****Solution:**

1 MB is 2^{20} bytes, and a byte is 2^3 bits, so $1\text{MB} = (2^{20} \text{ bytes}) (2^3 \text{ bits/byte}) = 2^{23} \text{ bits}$.

$16 \text{ MB} = 2^4 \text{ MB} = 2^{27} \text{ bits}$