

## CSCIU 210 – Computer Organization

### Homework-4, Weight: 30 points

**Due on Wednesday, October 17, 2018 at the beginning of the lecture (Hard Copy)**


*Note:* You need to include your calculation details to receive full credit!

**Q1. [10 points]** Draw the block symbol for a 8:1 MUX with two enables. Label the inputs as I<sub>0</sub>, I<sub>1</sub>, I<sub>2</sub>, ..., I<sub>7</sub>; select lines as S<sub>0</sub>, S<sub>1</sub>, S<sub>2</sub> and the output as F. The enables are E<sub>1</sub> and E<sub>2</sub>, where E<sub>1</sub> is active high and E<sub>2</sub> is active low.

**Q2. [10 points]** Draw the block symbol of a 2:4 decoder. Write the truth table for it, and draw the gate level circuit.

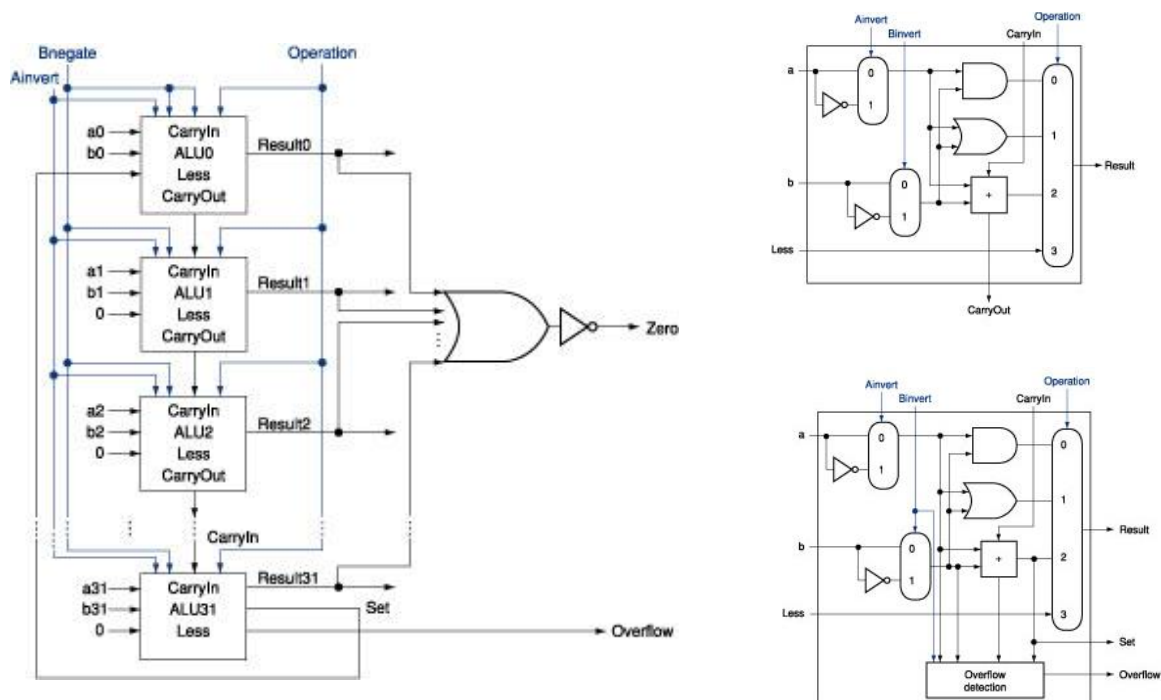**Q3. [10 points]** An ALU diagram we covered in class is shown below:

The ALU line control code is [Ainvert (1 bit), Binvert (1 bit), Operation (2 bit)]. Answer the following questions:



a) [5pts] Give ALU line code for NAND (not-AND) function

a) [5pts] Give ALU line code for SLT (set on less than) function