

Sample Exam 2

10-Nov-18

16 November 2018

Page 1/9

_____, _____
Last Name, First Name

Instructions:

- **Show all work on the front of the test papers. No work shown may mean 0 points given!** If you need more room, make a clearly indicated note on the front of the page, "MORE ON BACK", and use the back. The back of the page will **not** be graded without an indication on the front.
- **Read each question carefully and follow the instructions.** Unless otherwise stated, **you must show your work and clearly illustrate your steps.**
- If you round a numerical answer, you must give at least **3 significant digits.**
- Put your name at the top of **each** test page and be sure your exam consists of the number of pages designated in the headers.
- The space provided does **NOT** necessarily represent the amount of writing necessary.
- You may **not** use any notes, homework, labs, or other books. Only **memoryless** calculator is allowed.
- You may **not** use any notes, homework, labs, or other books.

COMMENTS, FEEDBACK, or any special instructions for the professor:

Problem	Available	Points
1		
2		
3		
4		
5		
Total		

Important: In completing this exam, I used a calculator with no communications capability, and no information of relevance to the course was stored in the calculator. I did not use any other electronic device or any other references. My work was solely my own.

Your Calculator's Maker and Model#: _____, Signature: _____

You must sign this to receive credit for the exam.

Important Boolean Algebra Laws

Identity law

- $A + 0 = A$
- $A \cdot 1 = A$

Zero and One laws

- $A + 1 = 1$
- $A \cdot 0 = 0$

Associative laws

- $A + (B + C) = (A + B) + C$
- $A \cdot (B \cdot C) = A \cdot (B \cdot C)$

Distributive laws

- $(B + C) = (A \cdot B) + (B \cdot C)$

- $A + (B \cdot C) = (A + B) \cdot (A + C)$

DeMorgan's laws

- $(A \cdot B)' = A' + B'$
- $(A + B)' = A' \cdot B'$

Inverse laws

- $A + A' = 1$
- $A \cdot A' = 0$

Commutative laws

- $A + B = B + A$
- $A \cdot B = B \cdot A$

Sample Exam 2

10-Nov-18

16 November 2018

Page 2/9

_____, _____
Last Name, First Name


Remember to show ALL work here and in EVERY problem on this exam.

Q1. What is a decoder? Construct a 3-to-8 decoder with basic gates. Clearly show all your steps with the truth table.

ANS:

A decoder is a combinational circuit that has 'n' inputs and ' 2^n ' outputs.

I ₂	I ₁	I ₀	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

 

Sample Exam 2


16 November 2018

10-Nov-18

Page 3/9

_____, _____
Last Name, First Name

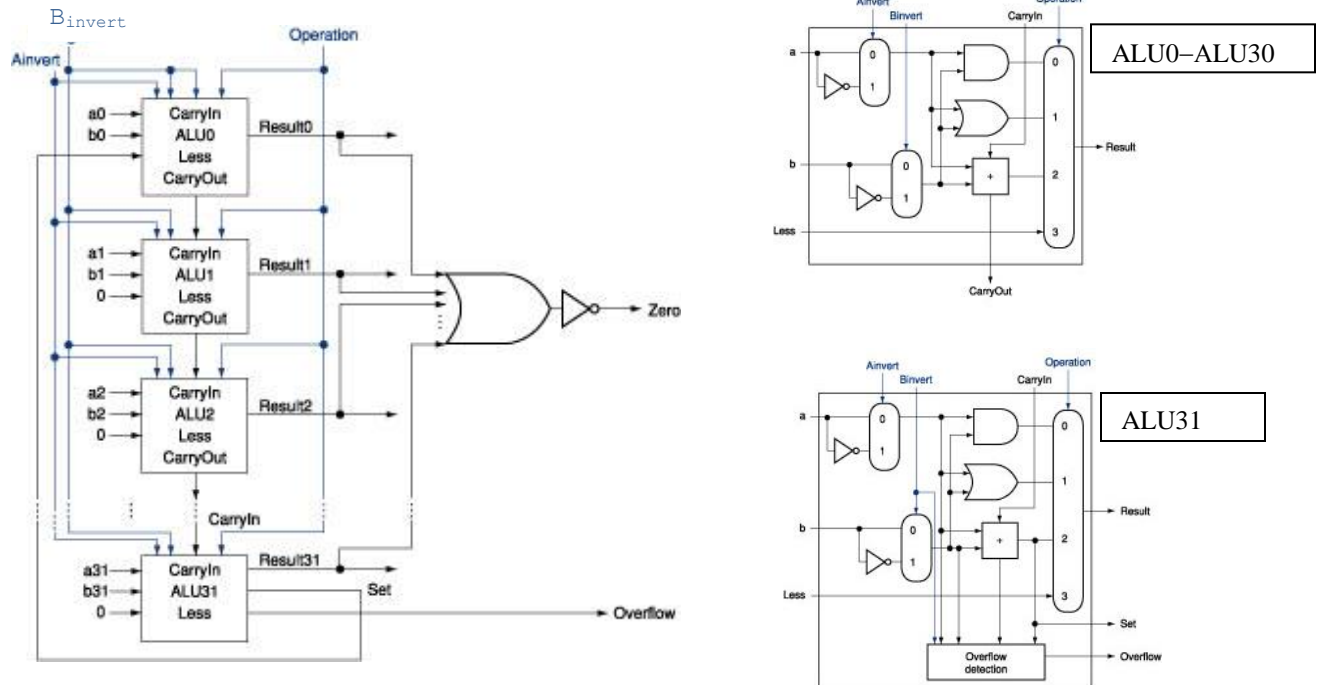Q2. The 32-bit ALU diagram we covered in class is attached below:



The ALU line control code is [A_{invert} (1 bit), B_{invert} (1 bit), Operation (2 bit)]. Answer the following questions:

a) Give ALU line code for OR function

Solution

0001

b) Give ALU line code for SUB (subtraction) function

Solution

0110

Sample Exam 2

10-Nov-18

16 November 2018

Page 4/9

_____, _____
Last Name, First Name

c) Assume

a = 00000000000000000111111111111111 and

b = 10000001110000000000000000000000.

Determine the ALU output after the ALU control code [0011] is executed. You need to give your reasoning which does not necessarily mean long calculation.

(Note: You don't have to give your result in the 32 bit format. If you can write your result with decimal number, it will be fine)

Solution

Since $a+b < 0$, ALU result is 1

- d) Under what kind of situation, this ALU will give wrong result for its SLT operation. Assume every component in this ALU is in good condition. (Note: when ALU executes SLT command, if $A < B$, then output should be 1)

Solution

When overflow happens

Sample Exam 2


16 November 2018

10-Nov-18

Page 5/9

_____, _____
Last Name, First Name

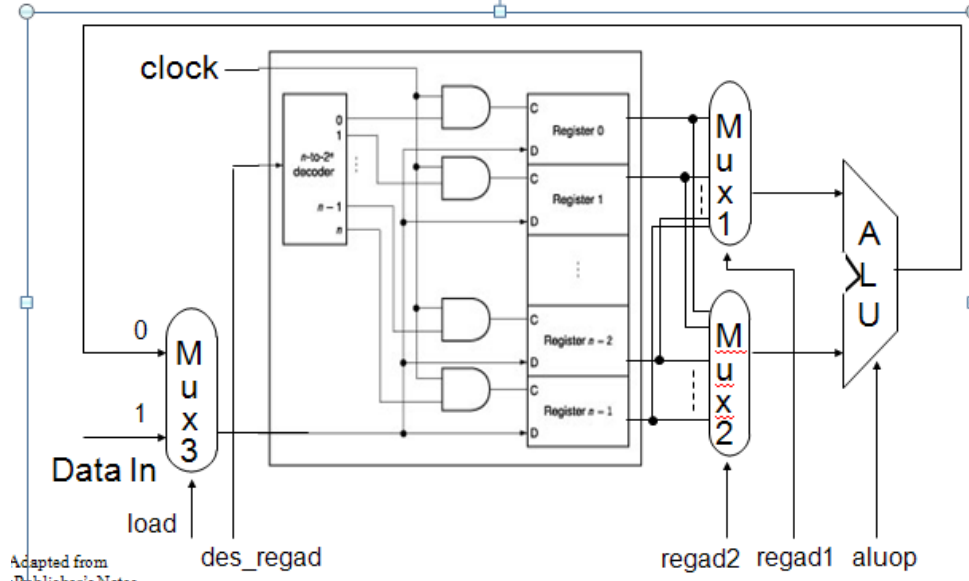Q3. A simple microprocessor diagram is illustrated below:



This processor's machine code format is [load, regad1, regad2, des_regad, aluop], where

load signal: 1 (read from external input), 0 (read from ALU)

regad1: the address of the register for the ALU input 1

regad2: the address of the register for the ALU input 2

des_regad: the address of the destination register which data is written into

aluop: the ALU function selection

Register number $r_0 \sim r_{15}$ (16 registers each of which has 16 bits)

ALU op code	ALU Function	Assembly Code
0 (000)	And	and
1 (001)	Or	or
2 (010)	NAND	nand
3 (011)	NOR	nor
4 (100)	XOR	xor
5 (101)	Addition	add
6 (110)	Subtraction	sub
7 (111)	Slt	slt

The syntax of assembly language of our simple processor is defined as following:

'sub r3, r1, r2' means: $r_3 = r_1 - r_2$, Machine Code: [0000100100011110]

'slt r3, r1, r2' means:

If $r_1 < r_2 \Rightarrow r_3 = 1$

Otherwise, $r_3 = 0$, Machine Code: [0000100100011111]

'load r5' means: external input data $\Rightarrow r_5$, Machine Code: [1XXXXXXXX0101XXX] (we assign all of 'X' equal to 0)

Based on the information above, answer the following questions:

Sample Exam 2

10-Nov-18

16 November 2018

Page 6/9

_____, _____
Last Name, First Name

- a) (True or False)
[T] In this processor, during each clock cycle, data from either ALU output or external data input will be written into one of its registers.
- b) Translate the assembly code 'add r1, r2, r3' to a machine code.

Solution

0001000110001101

- c) Translate the machine code [0110000111110011] back to an assembly code.

Solution

NOR, r14, r12, r3

- d) Someone writes a two line program for this computer as following:

```
0001100110011111
0001100110011010
```

Determine the content of register r3 as a 16 bit binary sequence after this program is executed assuming that each register has 16 bits.

Solution

These two lines are

```
slt r3, r3, r3      # set r3=0
nand, r3, r3, r3    #r3=1111111111111111
```

Sample Exam 2

10-Nov-18

16 November 2018

Page 7/9

_____, _____
Last Name, First Name

Q4. The following problem deal with transition from C to MIPS. Assume that the variables f, g, h, i, and j are assigned to registers \$s0, \$s1, \$s2, \$s3, and \$s4, respectively. Assume that the base address of the arrays A and B are in registers \$s6 and \$s7, respectively.

a.	$f = -g - A[6];$
b.	$B[4] = A[i - j];$

For the C statements above, (i) what is the corresponding MIPS assembly code? (ii) How many different registers are needed to carry out the C statement? (Need to work on case **a** and **b**)

(i)


a. lw \$s0, 24(\$s6)
sub \$s0, 0, \$s0
sub \$s0, \$s0, \$s1

b. sub \$t0, \$s3, \$s4
sll \$t0, \$t0, 2
add \$t0, \$s6, \$t0
lw \$t1, 0(\$t0)
sw \$t1, 16(\$s7)

(ii) **a. 3 and b. 6**

Q5. A D flip-flop output diagram is illustrated below. Assuming that (i) the initial value of Q is 0 and (ii) setup and hold time of D-type flip flop is zero, then, based on the clock and input waveform below, plot its output (Q) waveform.

ANS:

 

Sample Exam 2

10-Nov-18

16 November 2018

Page 8/9

_____, _____
Last Name, First Name

MIPS Instruction Formats:

Name	Fields					
Field Size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
R-Format	opcode	rs	rt	rd	shamt	funct
I-Format	opcode	rs	rt	address/immediate		
J-Format	opcode	target address				

MIPS Instructions:

Instruction	Type	opcode/funct (hex)*	Example	Meaning
add	R	0/20	add \$s1, \$s2, \$s3	$R[rd] = R[rs] + R[rt]$
addi	I	8	addi \$s1, \$s2, 100	$R[rt] = R[rs] + \text{SignExImm}$
and	R	0/24	and \$s1, \$s2, \$s3	$R[rd] = R[rs] \& R[rt]$
andi	I	c	andi \$s1, \$s2, 100	$R[rt] = R[rs] \& \text{ZeroExImm}$
beq	I	4	beq \$s1, \$s2, 25	If $(R[rs] == R[rt])$ $PC = PC + 4 + \text{Imm} * 4$
bne	I	5	bne \$s1, \$s2, 25	If $(R[rs] \neq R[rt])$ $PC = PC + 4 + \text{Imm} * 4$
j	J	2	j 2500	$PC = \text{jumpAddr}^{[1]}$
jal	J	3	jal 2500	$R[31] = PC + 4$; $PC = \text{jumpAddr}^{[1]}$
jr	R	0/8	jr \$ra	$PC = R[rs]$
lui	I	f	lui \$s1, 100	$R[rt] = \{ \text{imm}, 16 \text{ of } 0s \}$
lw	I	23	lw \$s1, 100(\$s2)	$R[rt] = \text{MEM}[R[rs] + \text{SignExImm}]$
nor	R	0/27	nor \$s1, \$s2, \$s3	$R[rd] = \sim(R[rs] R[rt])$
or	R	0/25	or \$s1, \$s2, \$s3	$R[rd] = R[rs] R[rt]$
ori	I	d	ori \$s1, \$s2, 100	$R[rt] = R[rs] \text{ZeroExImm}$
sll	R	0/0	sll \$s1, \$s2, 10	$R[rd] = R[rt] \ll \text{shamt}$
slt	R	0/2a	slt \$s1, \$s2, \$s3	$R[rd] = (R[rs] < R[rt]) ? 1 : 0$
slti	I	a	slti \$s1, \$s2, 100	$R[rt] = (R[rs] < \text{SignExImm}) ? 1 : 0$
srl	R	0/2	srl \$s1, \$s2, 10	$R[rd] = R[rt] \gg \text{shamt}$
sub	R	0/22	sub \$s1, \$s2, \$s3	$R[rd] = R[rs] - R[rt]$
sw	I	2b	sw \$s1, 100(\$s2)	$\text{MEM}[R[rs] + \text{SignExImm}] = R[rt]$

MIPS Register Convention:

Use	Number	Name
The constant 0	\$0	\$zero
Reserved for Assembler	\$1	\$at
Return Values	\$2-\$3	\$v0-\$v1
Arguments	\$4-\$7	\$a0-\$a3
Temporary	\$8-\$15	\$t0-\$t7
Saved Temporaries	\$16-\$23	\$s0-\$s7
Temporary	\$24-\$25	\$t8-\$t9
Used by Kernel	\$26-\$27	\$k0-\$k1
Global Pointer	\$28	\$gp
Stack Pointer	\$29	\$sp
Frame Pointer	\$30	\$fp
Return Address	\$31	\$ra

Sample Exam 2

10-Nov-18

16 November 2018

Page 9/9

_____, _____
Last Name, First Name

This Page Intentionally Left Blank