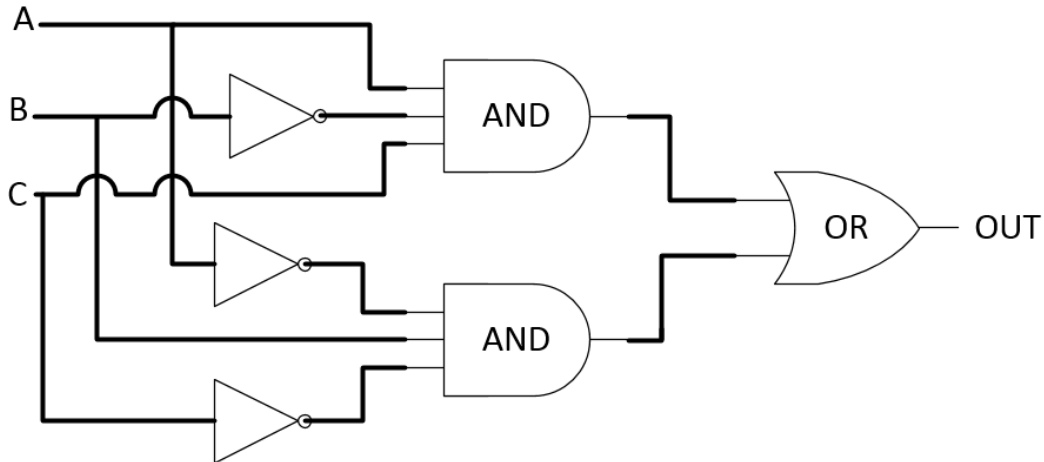


Instructions: You must show your work and put your final answers in the blanks. If you round a numerical answer, **you must give at least 3 significant digits**.

- 1) Convert the following Boolean equations to corresponding logic circuit using AND, OR, and NOT logic gates (ensure you label each input and output for every logic gate)

$$(A \cdot B' \cdot C) + (A' \cdot B \cdot C')$$

(Note: You can use three input logic gate in your diagram). [5 pts]



- 2) Perform the following number conversions [5 pts]

a) $1101.0011_2 = (\underline{\text{D.3}})_{16}$ (2 point)

b) $13.875_{10} = (\underline{1101.1110})_2$ (3 points)


Final Answer = (a) _____ (D.3)₁₆ _____, (b) _____ (1101.1110)₂ _____

Instructions: You must show your work and put your final answers in the blanks. If you round a numerical answer, **you must give at least 3 significant digits**.

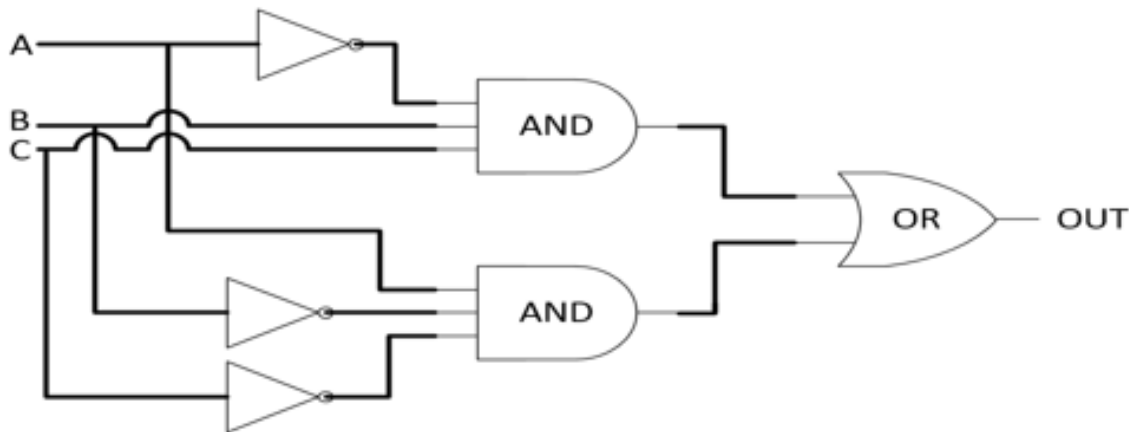- 3) Convert the following Boolean equations to corresponding logic circuit using AND, OR, and NOT logic gates (ensure you label each input and output for every logic gate)

$$(A' \cdot B \cdot C) + (A \cdot B' \cdot C')$$

(Note: You can use three input logic gate in your diagram). [5 pts]



Final Answer = _____

- 4) Perform the following number conversions [5 pts]

a) $32BD_{16} = (\underline{12989})_{10}$ (3 point)

$$32BD_{16} = 13 \times 16^0 + 11 \times 16^1 + 2 \times 16^2 + 3 \times 16^3 = 12989$$

b) $1011.0111_2 = (\underline{11.4375})_{10}$ (2 points)

Final Answer = (a) 12989, (b) 11.4375