
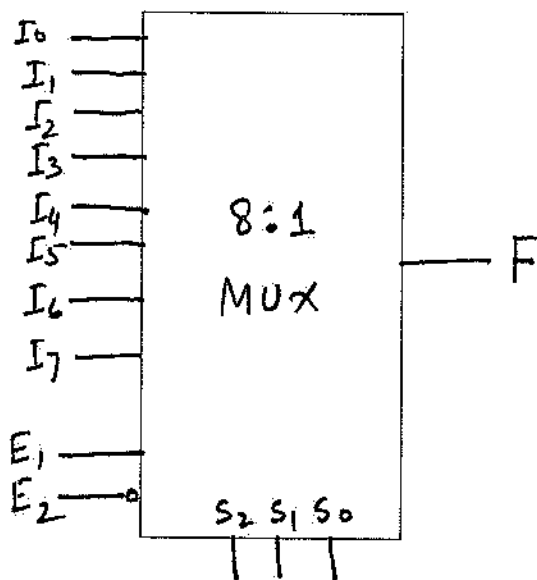


CSCIU 210 – Computer Organization**Homework-4Key, Weight: 30 points****Due on Wednesday, October 17, 2018 at the beginning of the lecture (Hard Copy)****Note:** You need to include your calculation details to receive full credit!

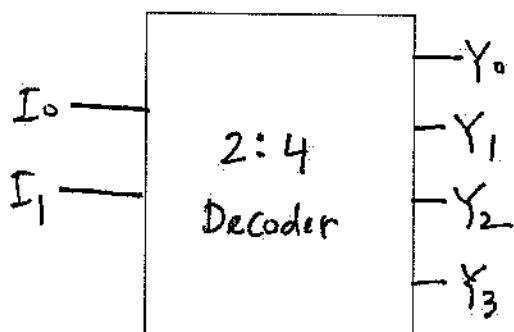
Q1. [10 points] Draw the block symbol for a 8:1 MUX with two enables. Label the inputs as $I_0, I_1, I_2, \dots, I_7$; select lines as S_0, S_1, S_2 and the output as F . The enables are E_1 and E_2 , where E_1 is active high and E_2 is active low.



Q2. [10 points] Draw the block symbol of a 2:4 decoder. Write the truth table for it, and draw the gate level circuit.





I_1	I_0	O_3	O_2	O_1	O_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

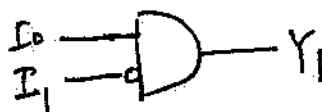

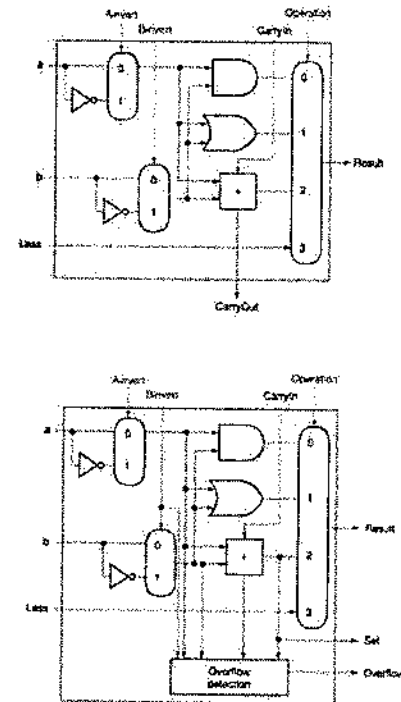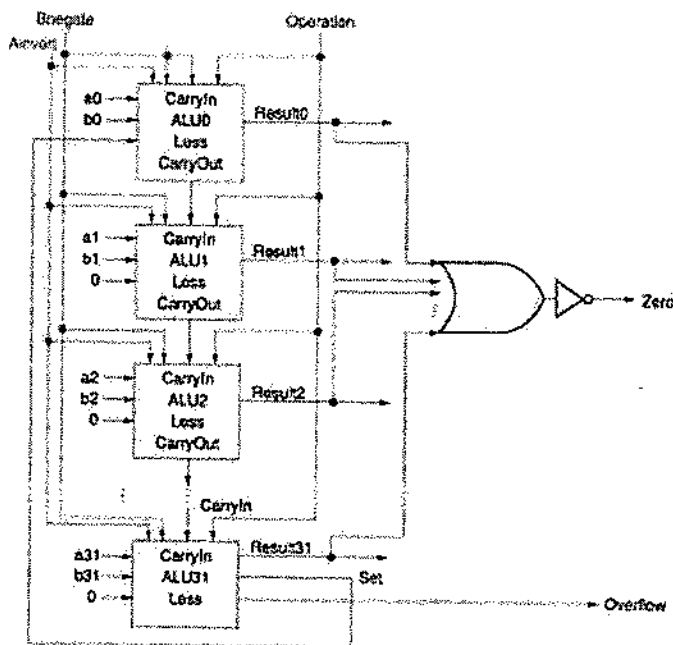Q3. [10 points] An ALU diagram we covered in class is shown below:

The ALU line control code is [Ainvert (1 bit), Binvert (1 bit), Operation (2 bit)]. Answer the following questions:



a) [5pts] Give ALU line code for NAND (not-AND) function

1101

b) [5pts] Give ALU line code for SLT (set on less than) function

0111